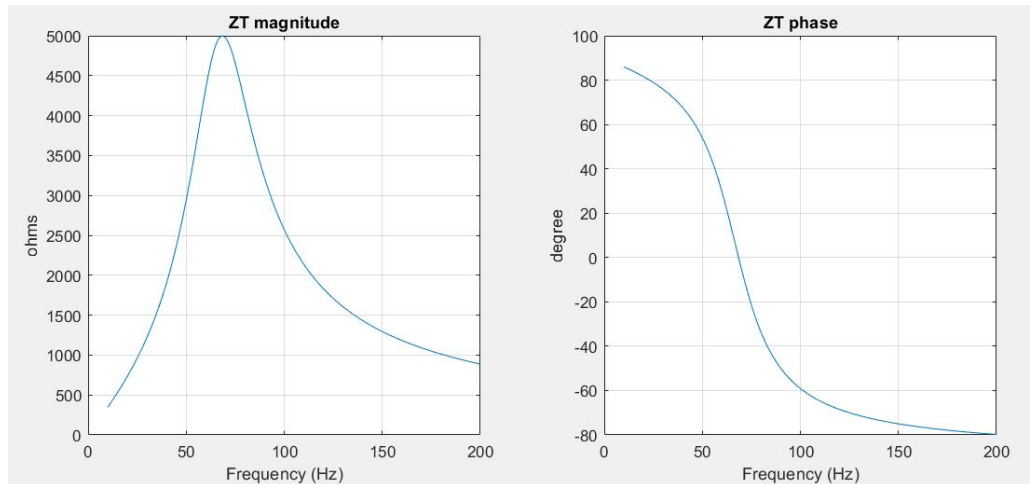


1. A parallel LRC circuit has $R = 5000$ ohms, $C = 1 \mu\text{F}$ and $L = 5.4$ henrys.

(a) Find the impedance, magnitude (ohms) and phase (degrees) and plot them versus frequency. (You should reproduce the graph below.)



$$Z_R = R = 5000 \text{ ohms}$$

$$Z_L = i\omega L = 5.4i\omega \text{ ohms}$$

$$Z_C = \frac{1}{i\omega C} = \frac{1000000}{i\omega} \text{ ohms}$$

$$Z_T = \frac{1}{\frac{1}{Z_R} + \frac{1}{Z_L} + \frac{1}{Z_C}} = \frac{1}{\frac{1}{R} + \frac{1}{i\omega L} + i\omega C} = \frac{R}{1 + \frac{R}{i\omega L} + i\omega CR} = \frac{R}{1 + \frac{iRC}{\omega}(\omega^2 - \omega_0^2)} \quad (\omega_0 = \frac{1}{\sqrt{LC}})$$

$$\text{magnitude } |Z_T| = \frac{R}{\sqrt{\left(\frac{RC}{\omega}(\omega^2 - \omega_0^2)\right)^2 + 1}} e^{i\varphi}$$

$$\text{phase } \varphi = -\arctan\left(\frac{RC}{\omega}(\omega^2 - \omega_0^2)\right)$$


(b) Confirm that the analytic value for Q (from class notes) is consistent with what you measure off the graph.

$$Q = R \sqrt{\frac{C}{L}} = 5000 \sqrt{\frac{1e-6}{5.4}} \approx 2.1517$$

$$Q = \omega_0 RC \quad (\omega_0 = 2\pi f)$$

$$Q = 2\pi * 68 * 5000 * 1e-6 \approx 2.1352$$

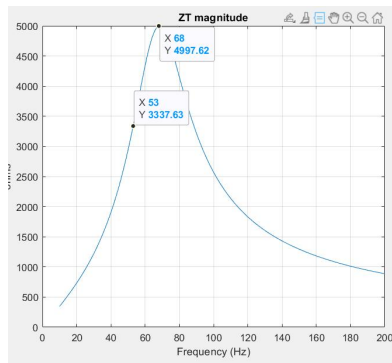Also, from this graph we can get f_0 and f_2 .



At $f_0(68)$, $|Z_T| = 4997.62$

At $f_2(53)$, $|Z_T| = 3337.63$ ($3337.62 * \sqrt{2} = 4720$)

$$\omega_0 = 2\pi f = 2\pi * 68 = 136\pi$$

$$\omega_2 = 2\pi * 53 = 108\pi$$

$$Q \equiv \frac{\omega_0}{2|\omega_2 - \omega_0|} = 2.26$$

The analytic value for Q is consistent with what we measure off the graph, within a reasonable margin of error.

2. a. Find the impedance, magnitude and phase, of this circuit in terms of L, C, R and ω ($\omega=2\pi f$, where f is the driving frequency in Hz.)

$$Z_C = \frac{1}{i\omega C}$$

$$Z_L = i\omega L$$

$$Z_R = R$$


$$Z_T = \frac{1}{\frac{1}{Z_R + Z_L} + \frac{1}{Z_C}} = \frac{1}{\frac{1}{R + i\omega L} + i\omega C} = \frac{R + i\omega L}{1 + (R + i\omega L)i\omega C} = \frac{R + i\omega L}{1 + i\omega CR - \omega^2 LC}$$

$$= \frac{R^2 + \omega^2 L^2}{R + i\omega(CR^2 - L + \omega^2 L^2 C)}$$

$$\text{magnitude } |Z_T| = \frac{R^2 + \omega^2 L^2}{[\sqrt{(\omega(CR^2 - L + \omega^2 L^2 C))^2 + R^2}]}$$

$$\text{phase } \varphi = -\arctan(\omega(CR^2 - L + \omega^2 L^2 C)/R)$$

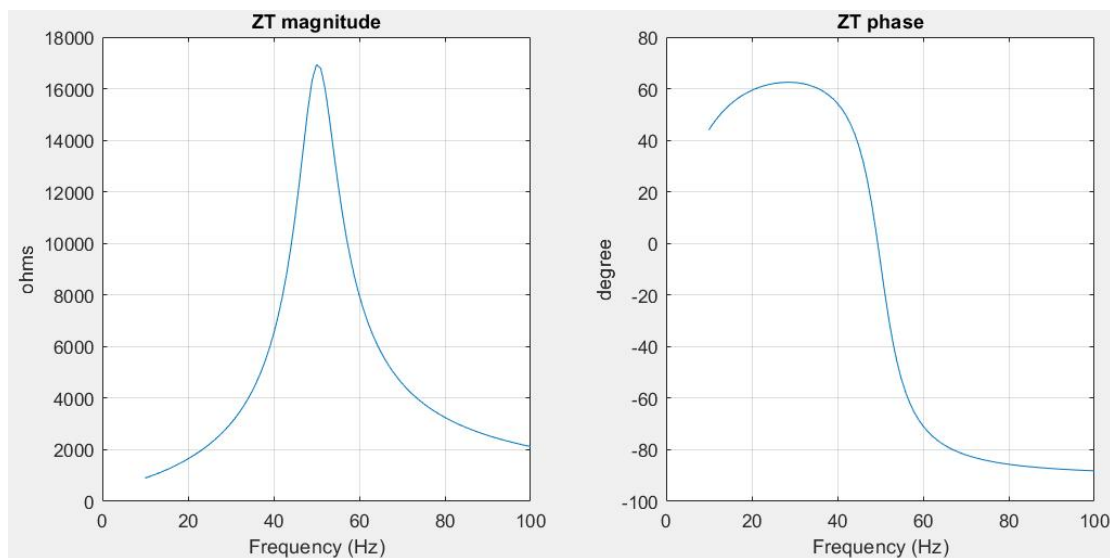b. Plot Z (mag and phase (in degrees)) for R=600 ohms, C= 1 μ F and L = 10 henrys. Plot the result for frequency from 10 to 100 Hz.



c. Show analytically that the Q of this circuit $\approx (1/R)\sqrt{L/C}$. (See lecture notes for hints.)

$$|Z_T| = \frac{R^2 + \omega^2 L^2}{\sqrt{(\omega(CR^2 - L + \omega^2 L^2 C))^2 + R^2}}$$

when $\omega = \omega_0$, $|Z_T|$ max occurs.

$$|Z_T|_{\text{max}} = \frac{R^2 + \omega_0^2 L^2}{\sqrt{(\omega_0(CR^2 - L + \omega_0^2 L^2 C))^2 + R^2}}$$

$$\text{plug in } \omega_0 = \frac{1}{\sqrt{LC}}$$

$$|Z_T|_{\text{max}} = \frac{R^2 + \frac{L}{C}}{R \sqrt{\frac{CR^2 + L}{L}}} = \frac{\sqrt{CLR^2 + L^2}}{CR}$$

when $\omega = \omega_2$, $|Z_T| = |Z_T|_{\max}/\sqrt{2}$.

$$\frac{R^2 + \omega_2^2 L^2}{\sqrt{(\omega_2(CR^2 - L + \omega_2^2 L^2 C))^2 + R^2}} = \frac{\sqrt{CLR^2 + L^2}}{\sqrt{2}CR}$$

$$\omega_2 = \frac{2\sqrt{LC} \pm RC}{2LC}$$

$$|\omega_2 - \omega_0| = \frac{R}{2L}$$


$$Q \equiv \frac{\omega_0}{2|\omega_2 - \omega_0|} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$\text{therefore, } Q \cong \frac{1}{R} \sqrt{\frac{L}{C}}$$

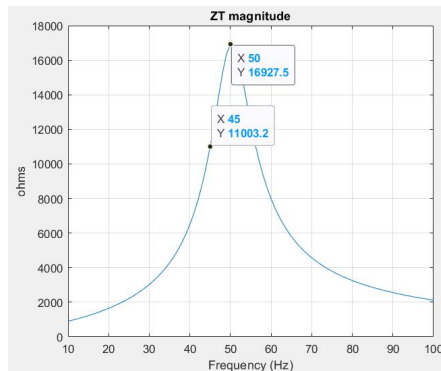d. Show that this makes sense based on measuring Q from your plots in (b).

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{600} \sqrt{\frac{10}{1e-6}} \approx 5.27$$

From this graph, we can get f_0 and f_2 .



At $f_0(50)$, $|Z_T| = 16927.5$

At $f_2(45)$, $|Z_T| = 11003.2$ ($11003.2 * \sqrt{2} = 15560.9$)

$$\omega_0 = 2\pi f = 2\pi * 50 = 100\pi$$

$$\omega_2 = 2\pi * 45 = 90\pi$$

$$Q \equiv \frac{\omega_0}{2|\omega_2 - \omega_0|} = 5$$